

# EE3900:Linear Systems and Signal Processing

## Lab Report

Lokesh Badisa  
AI21BTECH11005

Nov 2022

# Outline


- 1 Cover Page
- 2 Apparatus
- 3 Circuit Diagram
- 4 Waveforms

# Cover


- Title: Working Model of Mobile Charger
- Date: 4-5 Segment of 3<sup>rd</sup> segment
- Team/Individual Project: Individual Project
- Course: EE3900

- BreadBoard or PCB
- Transformer(12V-0-12V)
- 7805 Regulator
- Diodes(4)
- 100F Capacitor
- Connecting Wires
- Soldering Equipment


# Circuit Diagram

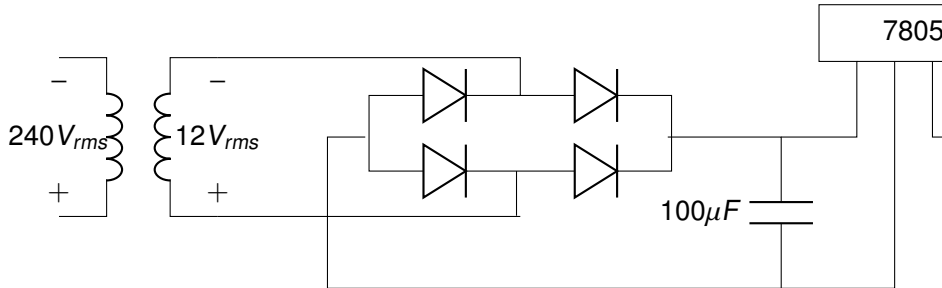


# Input Waveforms: 18V Peak

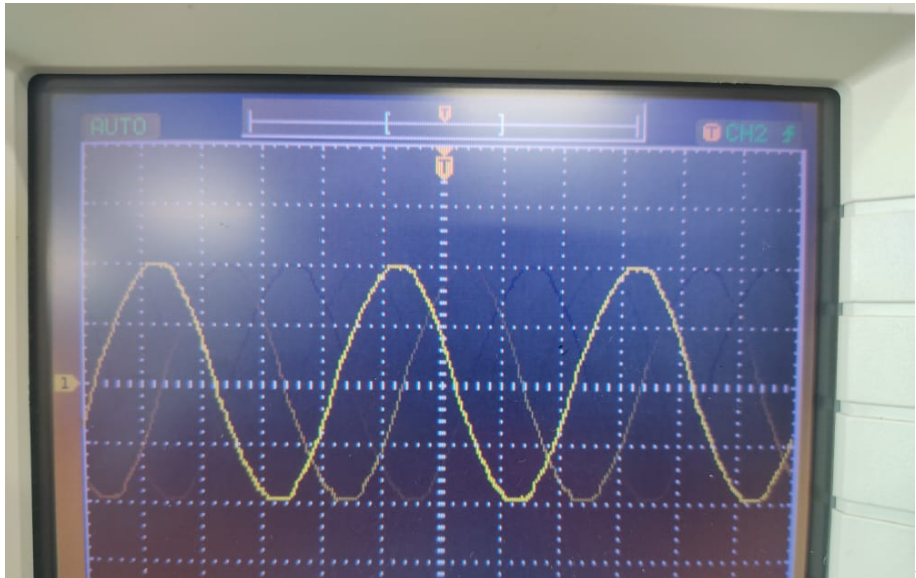

# Output Waveform: Constant 5V

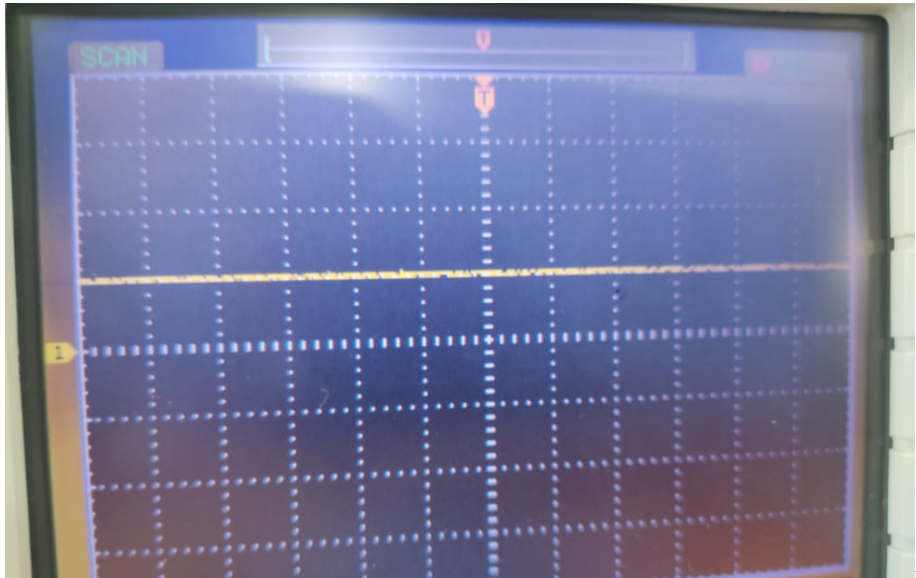

# Half-Wave Rectified Waveform: Peak 18V

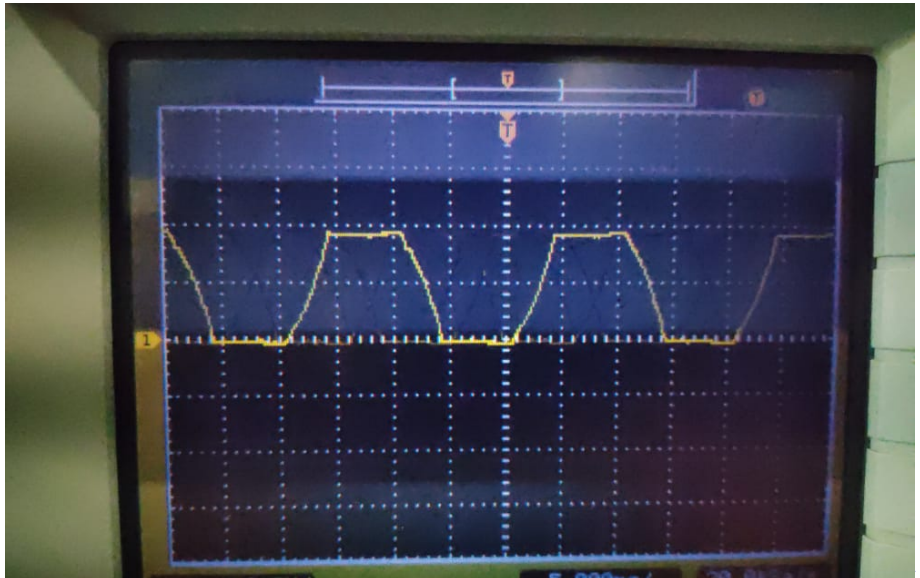



# Output DC Waveform at Filter Stage: Constant 18V

